

---

# Computational Microelectronics L2

Sung-Min Hong

[smhong@gist.ac.kr](mailto:smhong@gist.ac.kr)

Semiconductor Device Simulation Laboratory, GIST

---

# Binary adder

# Addition of binary numbers

---

- We can recognize that
  - Addition of two 1-bit binary numbers is the core operation.
  - There are only *four* possible cases.

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$



Carry



# Inclusion of carry-bit

- We introduce a separate bit for representing the carry.
  - Carry-bit & sum-bit

$$\begin{array}{rcl} 0 + 0 & = & 00 \\ 0 + 1 & = & 01 \\ 1 + 0 & = & 01 \\ 1 + 1 & = & 10 \end{array}$$

Carry

Sum

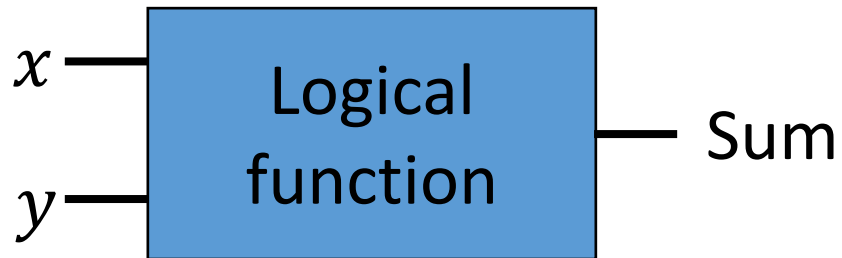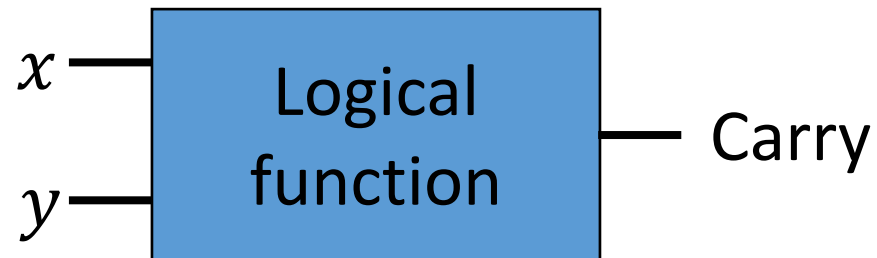

# Truth tables

---

- Relation between  $x$ ,  $y$ , and the output

– Sum-bit

$x \text{ XOR } y$

$x$	$y$	sum
0	0	0
0	1	1
1	0	1
1	1	0

– Carry-bit

$x \text{ AND } y$

$x$	$y$	carry
0	0	0
0	1	0
1	0	0
1	1	1



---

# Compact MOSFET model
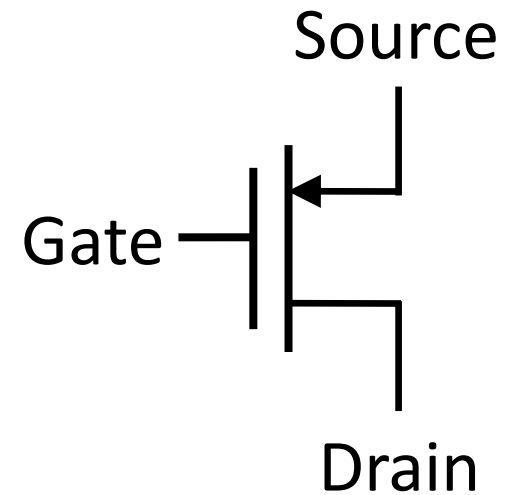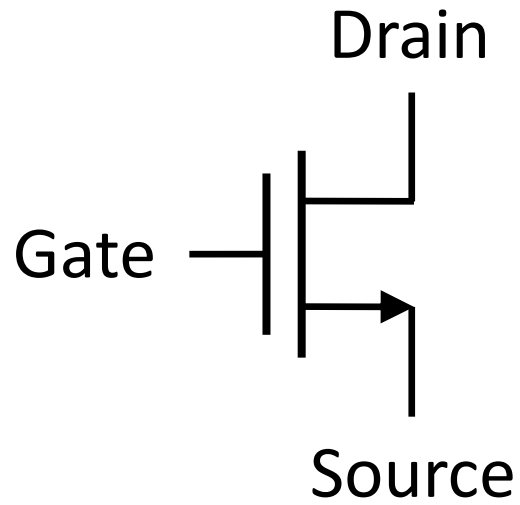
# MOSFET

---

- Basic unit of microelectronics
  - Controlled by the gate voltage
  - NMOSFET and PMOSFET



# Level 1 model (NMOSFET)

---

- A simple model (Shichman-Hodges)

- Its basic current model is:

- Cutoff region,  $V_{gs} < V_t$

$$I_d = 0$$

- Linear region,  $V_{ds} < V_{gs} - V_t$

$$I_d = \textcolor{red}{KP} \frac{W_{eff}}{L_{eff}} (1 + \textcolor{red}{LAMBDA} \times V_{ds}) \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

- Saturation region,  $V_{ds} > V_{gs} - V_t$

$$I_d = \frac{\textcolor{red}{KP}}{2} \frac{W_{eff}}{L_{eff}} (1 + \textcolor{red}{LAMBDA} \times V_{ds}) (V_{gs} - V_t)^2$$

- (Red-colored quantities are the SPICE model parameters.)



# Level 1 model (NMOSFET)

---

- A simple model (Shichman-Hodges)

- Threshold voltage:

- For nonnegative  $V_{sb}$ ,

$$V_t = VTO + GAMMA \left( \sqrt{PHI + V_{sb}} - \sqrt{PHI} \right)$$

- $VTO$  is the “zero-bias” threshold voltage.

- $GAMMA$  is the body effect coefficient.


- $PHI$  is the surface potential.

# NMOSFET example

- Consider the following parameters:

$KP=155e-6$   $LAMBDA=0.2$   $VTO=0.4$   $PHI=0.93$   $GAMMA=0.6$

$$-W_{eff}/L_{eff} = 2$$

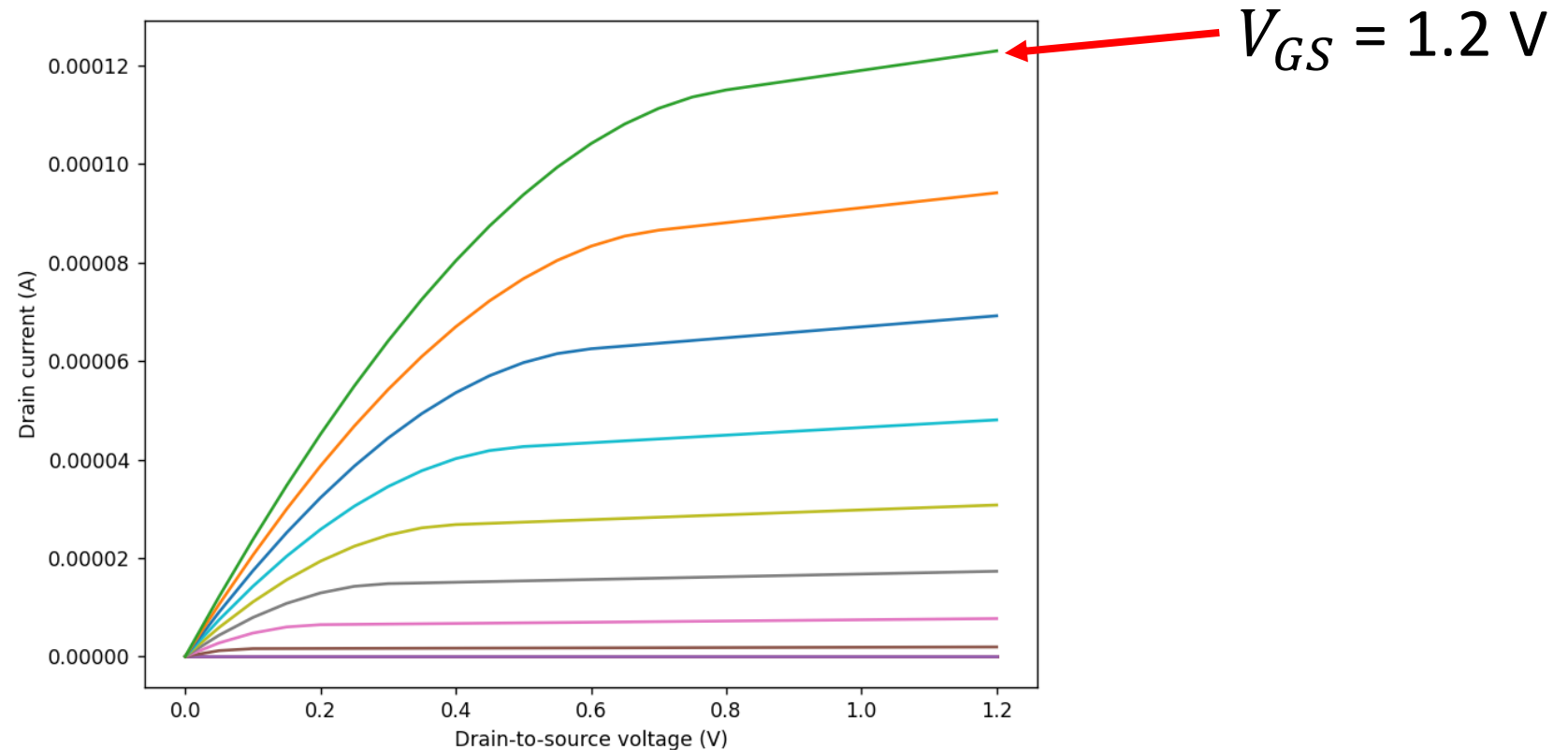


# PMOSFET example

- Consider the following parameters:

$KP=80e-6$   $LAMBDA=0.2$   $VTO=-0.4$   $PHI=0.93$   $GAMMA=0.6$

$$-W_{eff}/L_{eff} = 2$$

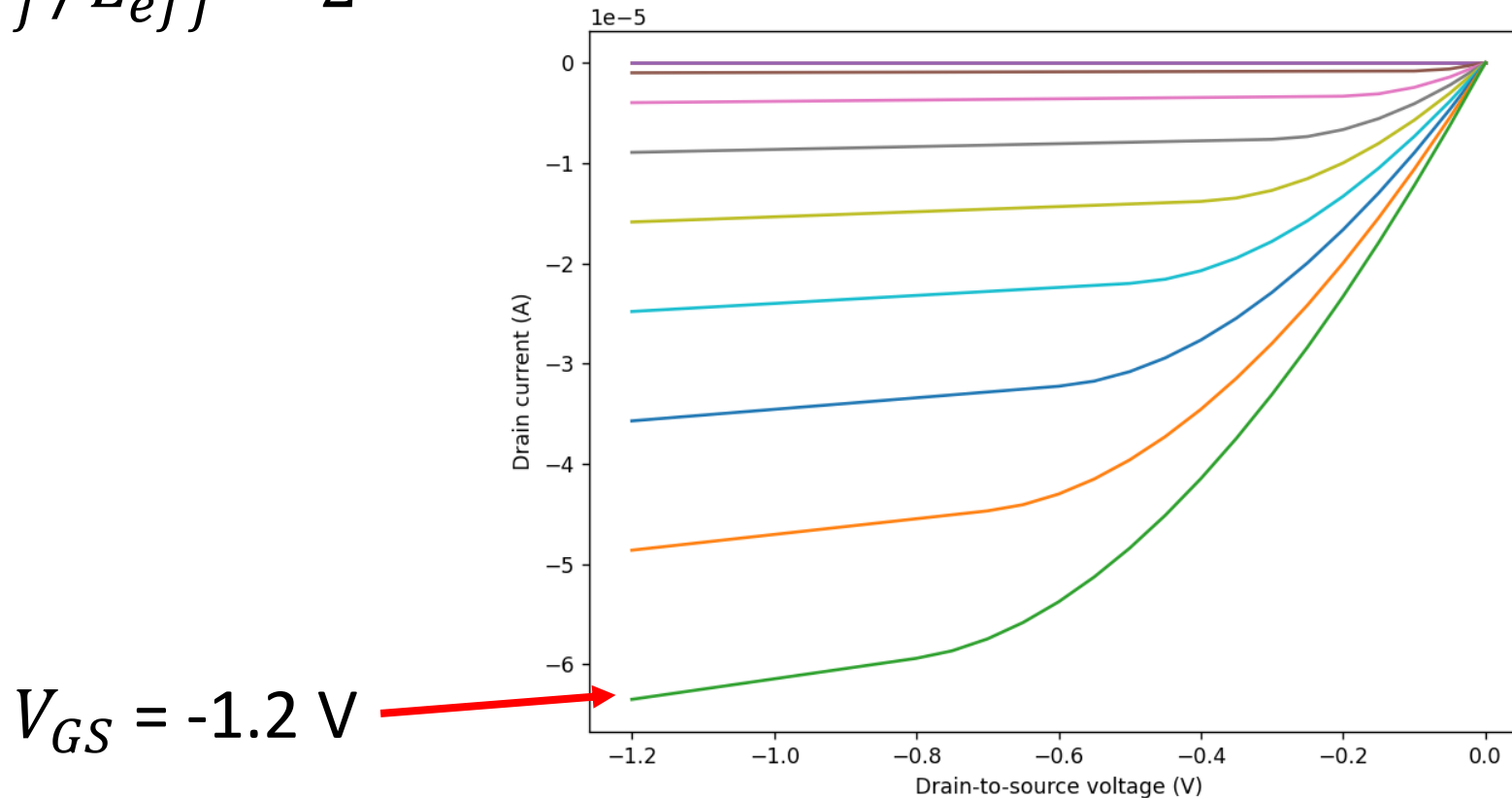


---

# CMOS inverter
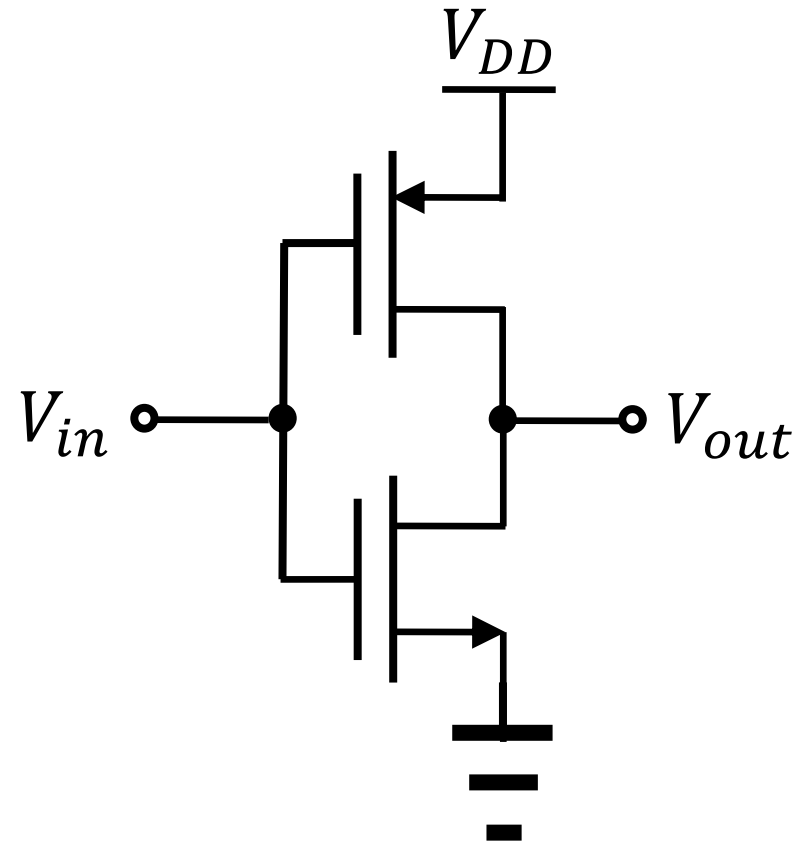
# The simplest logic gate

- When  $V_{in} = 0$ ,
  - NMOS OFF
  - PMOS ON
  - $V_{out}$  is “pulled up.”
  - $V_{out} = V_{DD}$
- When  $V_{in} = V_{DD}$ ,
  - NMOS ON
  - PMOS OFF
  - $V_{out}$  is “pulled down.”
  - $V_{out} = 0$



# Assume that $V_{in}$ is given.


---

- The goal is to calculate  $V_{out}$ .
  - $V_{out}(V_{in})$  is called the voltage transfer curve.

- What is the condition for a point on the VTC?

$$I_{Dn} + I_{Dp} = 0$$

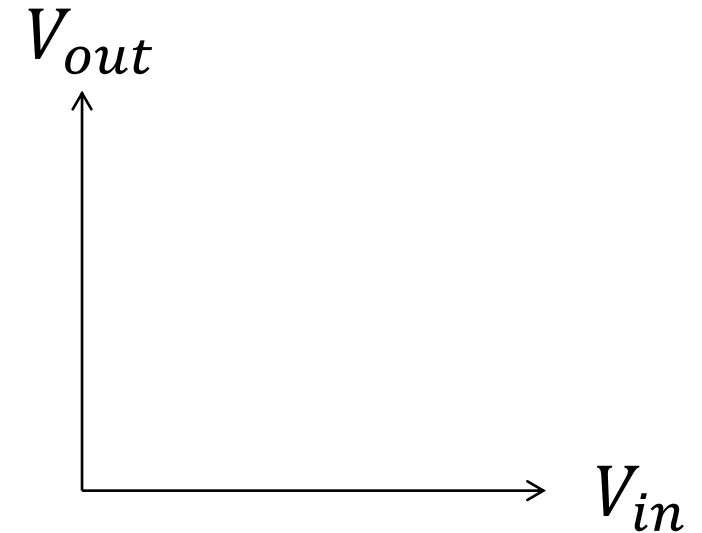- Assume that  $V_{DD} = 1.2$  V.
  - For example, at  $V_{in} = 0.5$  V and  $V_{out} = 0.7$  V, we have  $I_{Dn} = 1.77$   $\mu$ A and  $I_{Dp} = -7.92$   $\mu$ A. Certainly, it is not on the VTC.




# One possible way (Trial-and-error)

---

- In order to increase  $I_{Dn}$ , we can try a higher  $V_{out}$ , for example 0.8 V.
  - Still, the currents are much different.
  - 0.9 V. No.
  - 1.0 V. No.
  - 1.1 V. No.
  - 1.2 V. Well, now,  $I_{Dn} = 1.92 \mu\text{A}$  and  $I_{Dp} = 0 \text{ A}$ . We must increase  $|I_{Dp}|$ .
  - 1.15 V.  $I_{Dn} = 1.91 \mu\text{A}$  and  $I_{Dp} = -2.22 \mu\text{A}$ . We must increase  $I_{Dn}$ .
  - 1.175 V.  $I_{Dn} = 1.91 \mu\text{A}$  and  $I_{Dp} = -1.16 \mu\text{A}$ . We must increase  $|I_{Dp}|$ .
  - 1.1625 V.  $I_{Dn} = 1.91 \mu\text{A}$  and  $I_{Dp} = -1.70 \mu\text{A}$ . We are getting closer...
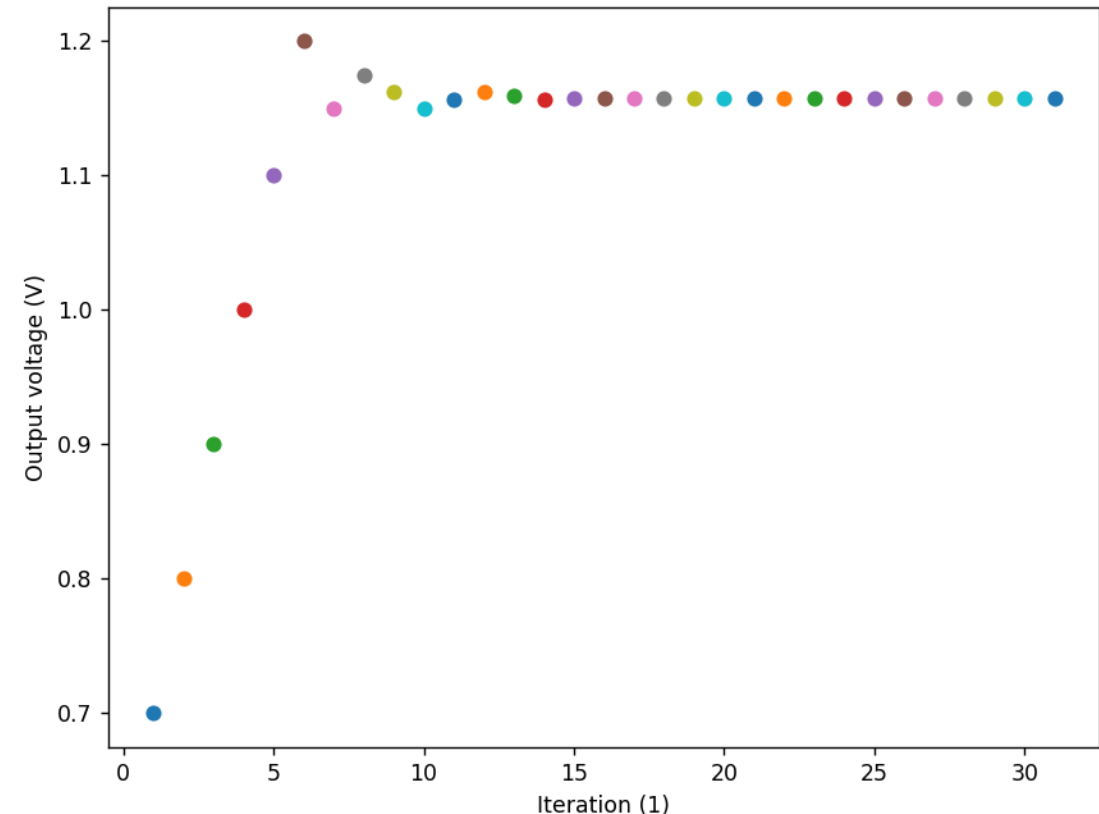
# Number of iterations

- When we have a voltage change smaller than 1  $\mu\text{V}$ , the calculation stops.
  - Start at  $\frac{V_{DD}}{2}$ .
  - Initial step is 0.1 V.
  - When the sign of difference changes, the step is reduced with a factor of 0.5. Otherwise, keep the step.
  - 31 iterations at  $V_{in} = 0.5 \text{ V}$





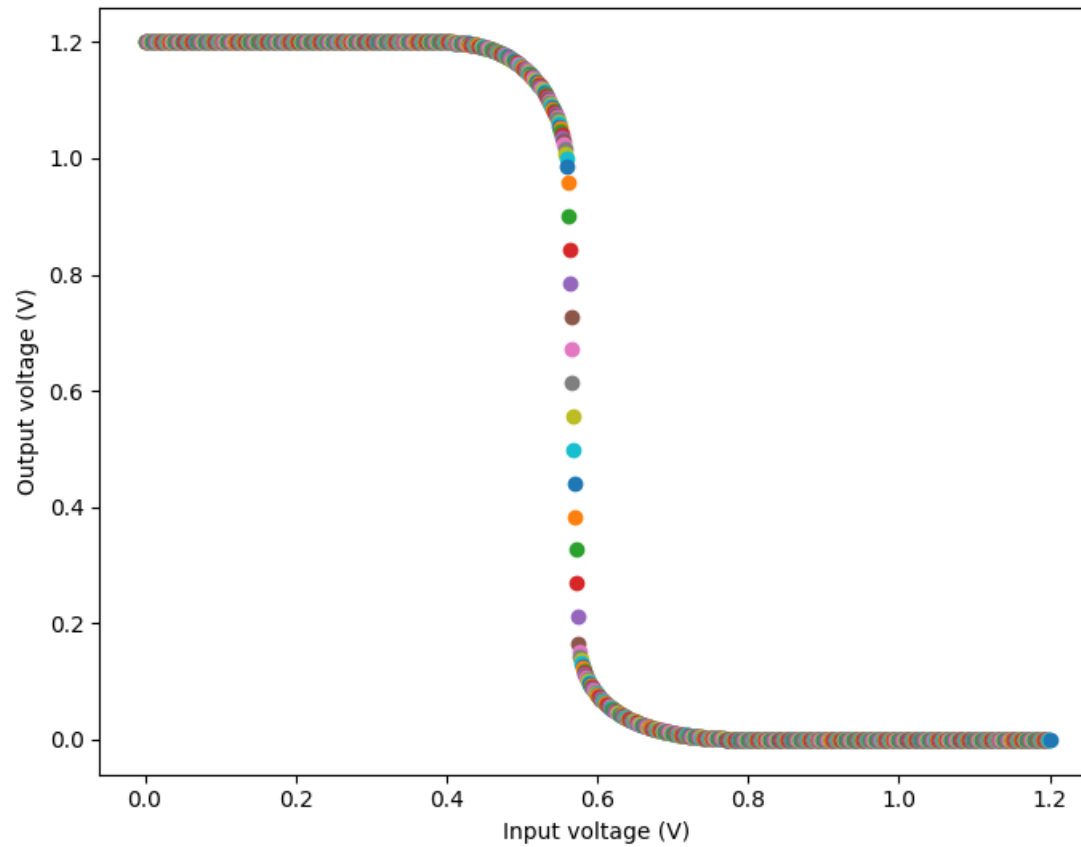
# Homework#2

---

- Due: AM08:00, September 19 (Two weeks later)
- Problem#1
  - Draw the voltage transfer curve.



---

**Thank you for your attention!**