
Computational Microelectronics

L12

Sung-Min Hong

smhong@gist.ac.kr

Semiconductor Device Simulation Laboratory, GIST

Transient simulation


RC circuit

- Consider a series RC circuit.
 - It is driven by a voltage source, $V_{in}(t)$. For $t < 0$, it was zero.

$$\frac{V_X - V_{in}(t)}{R} + C \frac{dV_X}{dt} = 0$$

- At $t = 0$, $V_{in}(t)$ is suddenly ramped up to V_{DD} ,
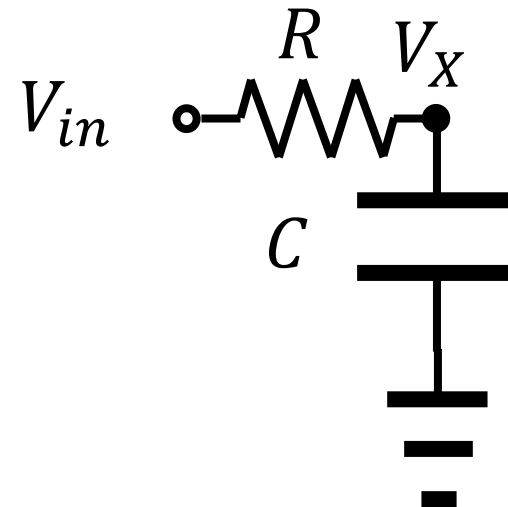
$$V_X(t) = V_{DD} \left[1 - \exp\left(-\frac{t}{RC}\right) \right]$$



Euler schemes

- Forward Euler scheme

- In the forward Euler scheme, the time derivative is calculated by taking the difference between the **future** and **present** values:

$$\left. \frac{\partial C(x_i)}{\partial t} \right|_{t_k} \approx \frac{C(t_{k+1}) - C(t_k)}{t_{k+1} - t_k}$$

- Backward Euler scheme

- In the backward Euler scheme, the time derivative is calculated by taking the difference between the **present** and **past** values:

$$\left. \frac{\partial C(x_i)}{\partial t} \right|_{t_k} \approx \frac{C(t_k) - C(t_{k-1})}{t_k - t_{k-1}}$$

Backward Euler

- Let us assume a constant time step, Δt .
 - At $t_i = i\Delta t$ ($i \geq 1$), the KCL can be discretized as

$$\frac{V_X(t_i) - V_{in}(t_i)}{R} + C \frac{V_X(t_i) - V_X(t_{i-1})}{\Delta t} = 0$$

- After a simple manipulation,

$$\left(1 + \frac{\Delta t}{RC}\right) V_X(t_i) = V_X(t_{i-1}) + \frac{\Delta t}{RC} V_{in}(t_i)$$

- For our present example, $V_{in}(t_i)$ is always V_{DD} .

$R = C = V_{DD} = 1$

- Assume that R is 1 Ω , C is 1 F, and V_{DD} is 1 V.

- In this case, the equation is simply written as



$$(1 + \Delta t)V_X(t_i) = V_X(t_{i-1}) + \Delta t$$

- Its analytic solution is

$$V_X(t_i) = 1 - \exp(-t_i)$$



Case study) $\Delta t = 1$

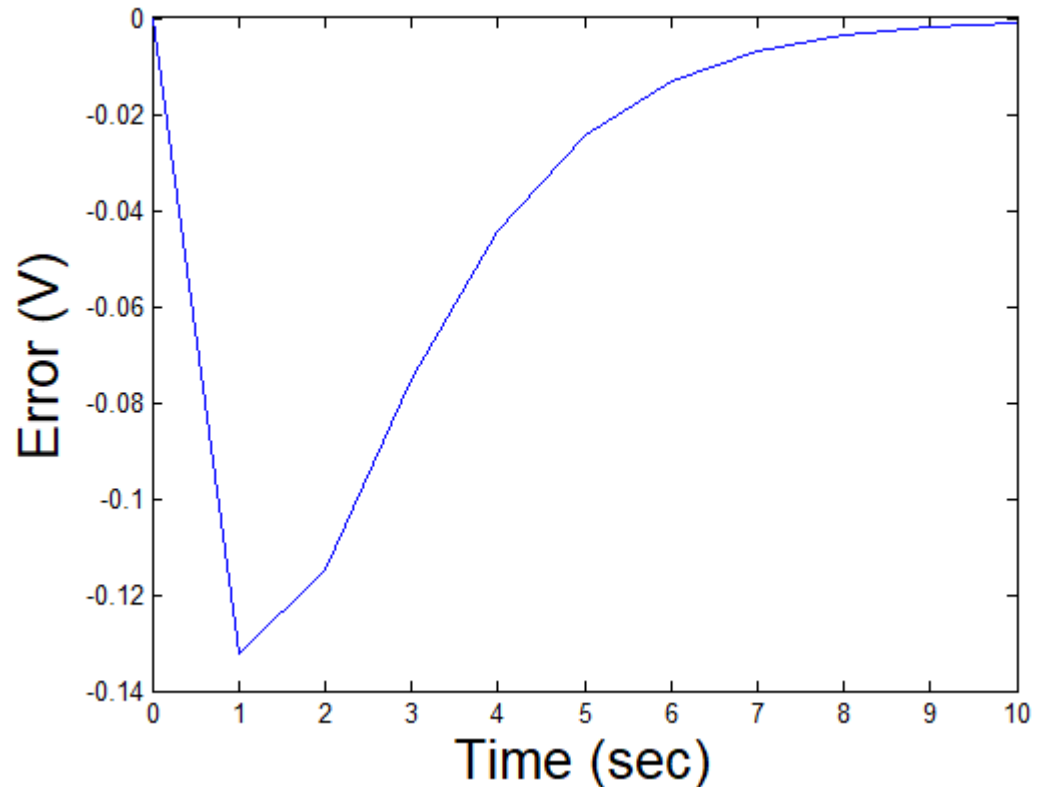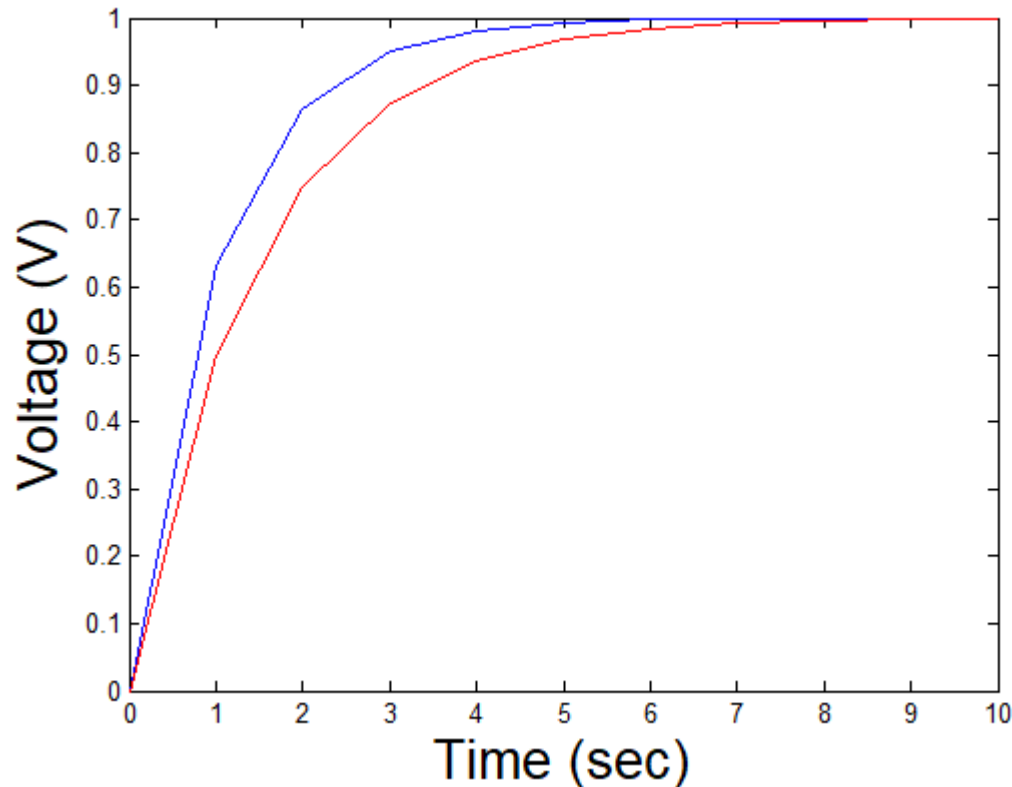- Run the simulation up to 10 sec.
 - Exact solution (blue curve in left figure), numerical solution (red curve in left figure), and error (right figure)





Case study) $\Delta t = 0.1$

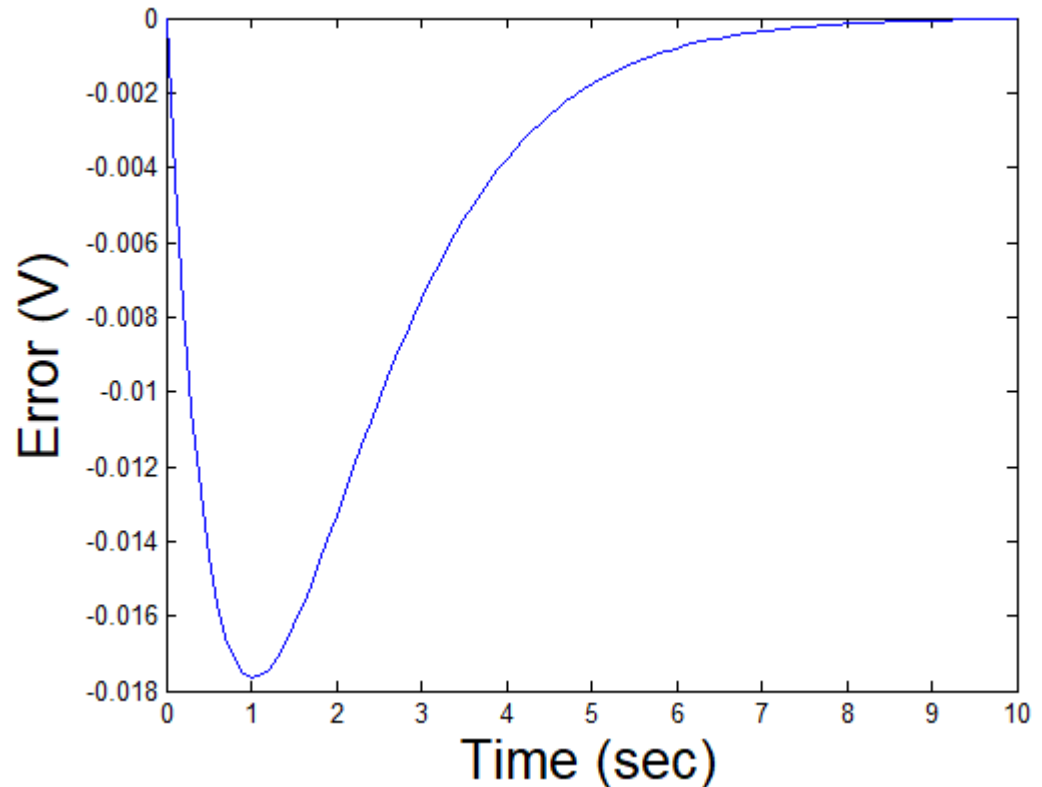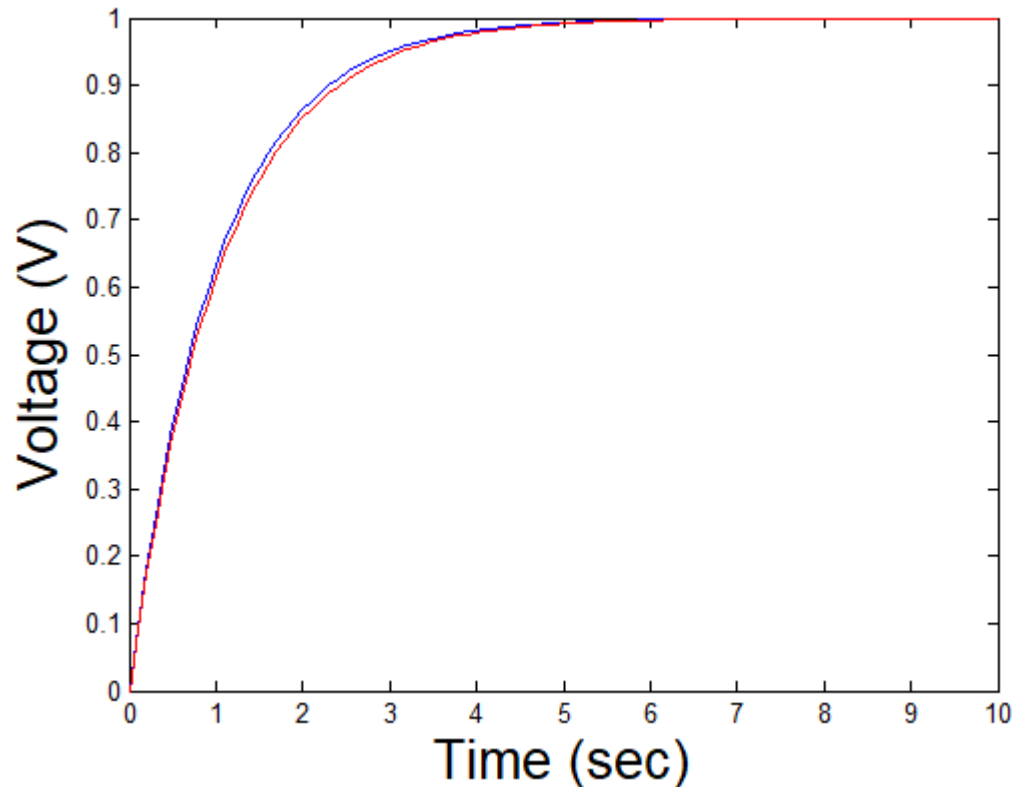- Ten times shorter time spacing
 - It looks much better.
 - Still, we have the maximum difference larger than 0.01 V.



Case study) $\Delta t = 0.01$

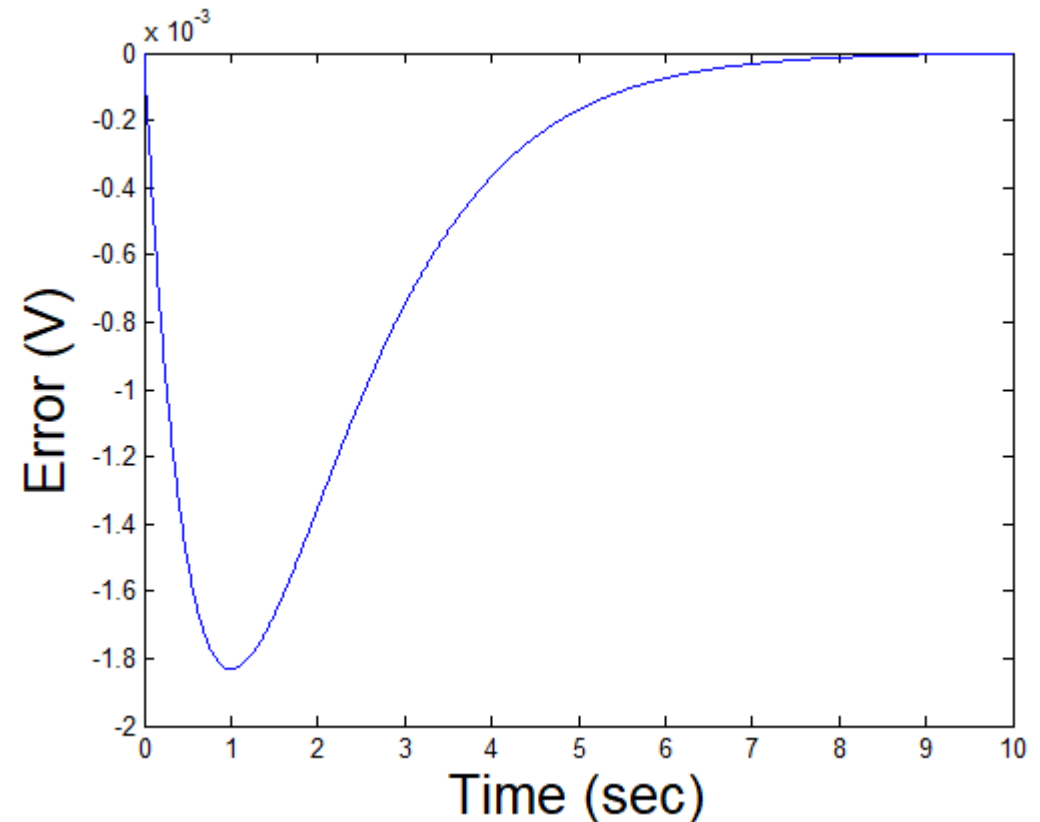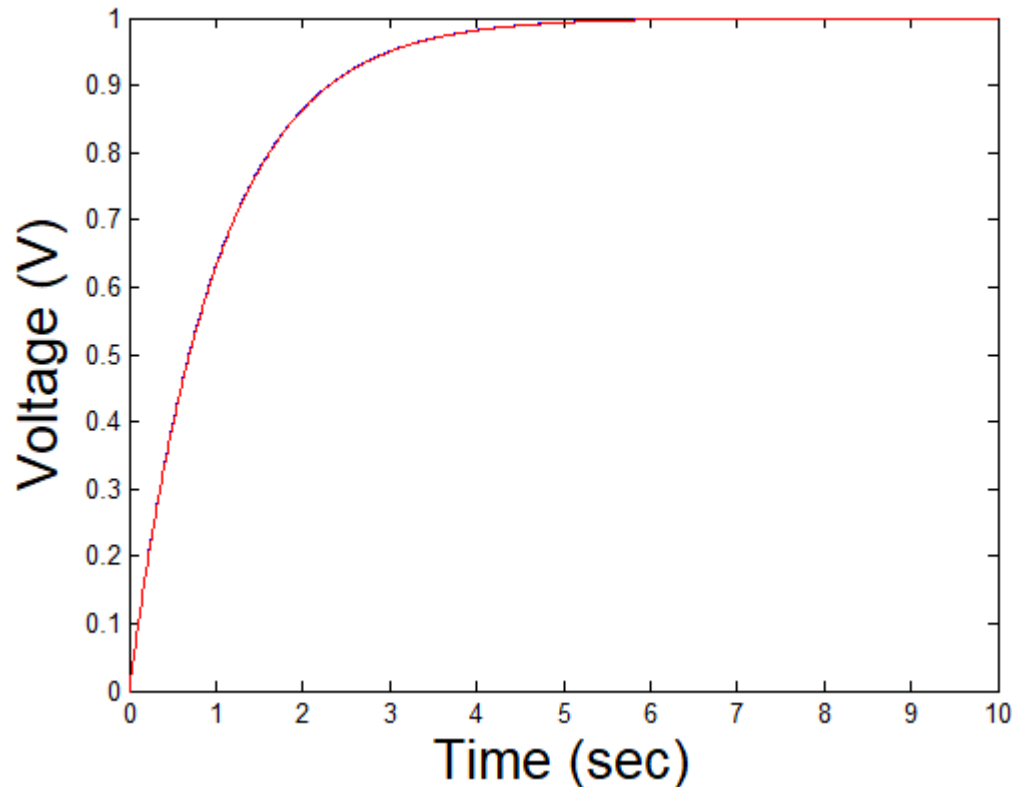- Ten times shorter time spacing, again
 - The difference becomes almost invisible.
 - The error is ten times smaller than that of $\Delta t = 0.1$.



Another method

- Gear's 2nd order method
 - Assume a constant time spacing, Δt .
 - Then, for $i \geq 2$,

$$\left. \frac{\partial f}{\partial t} \right|_{t_i} \approx \frac{1.5f(t_i) - 2f(t_{i-1}) + 0.5f(t_{i-2})}{\Delta t}$$

- For $i = 1$, just use the backward Euler method.
- It means that

$$\frac{V_X(t_i) - V_{in}(t_i)}{R} + C \frac{1.5V_X(t_i) - 2V_X(t_{i-1}) + 0.5V_X(t_{i-2})}{\Delta t} = 0$$

After re-arranging terms,



- A slightly different expression for $V_X(t_i)$
 - Compare it against the backward Euler:

$$(1.5 + \Delta t)V_X(t_i) = 2V_X(t_{i-1}) - 0.5V_X(t_{i-2}) + \Delta t$$

$$(1 + \Delta t)V_X(t_i) = V_X(t_{i-1}) + \Delta t$$



Case) $\Delta t = 1$ with Gear's method

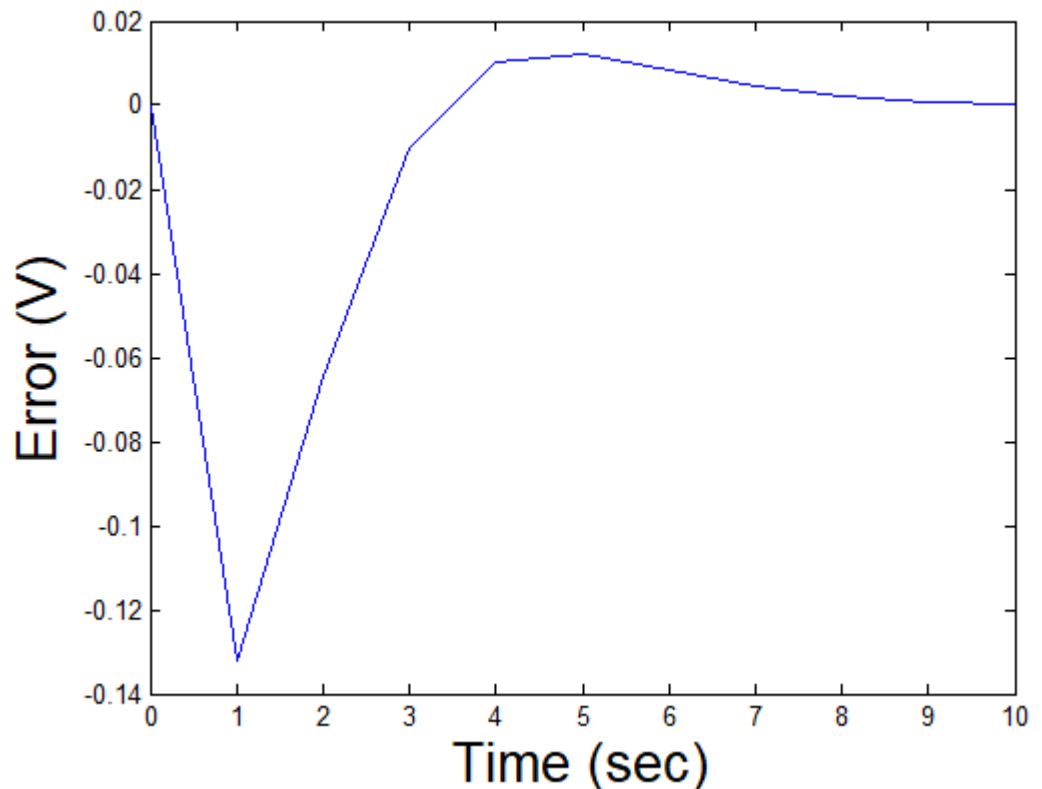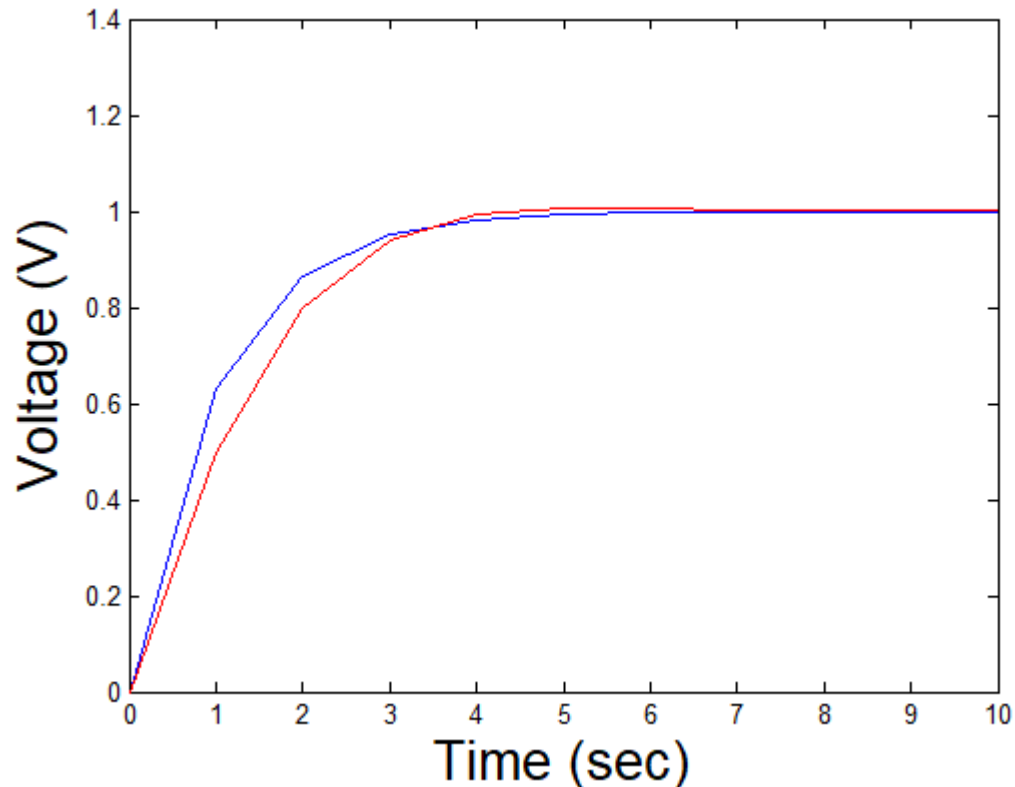- Run the simulation up to 10 sec, again.
 - The maximum error is determined by the first backward Euler step.





Case) $\Delta t = 0.1$ with Gear's method

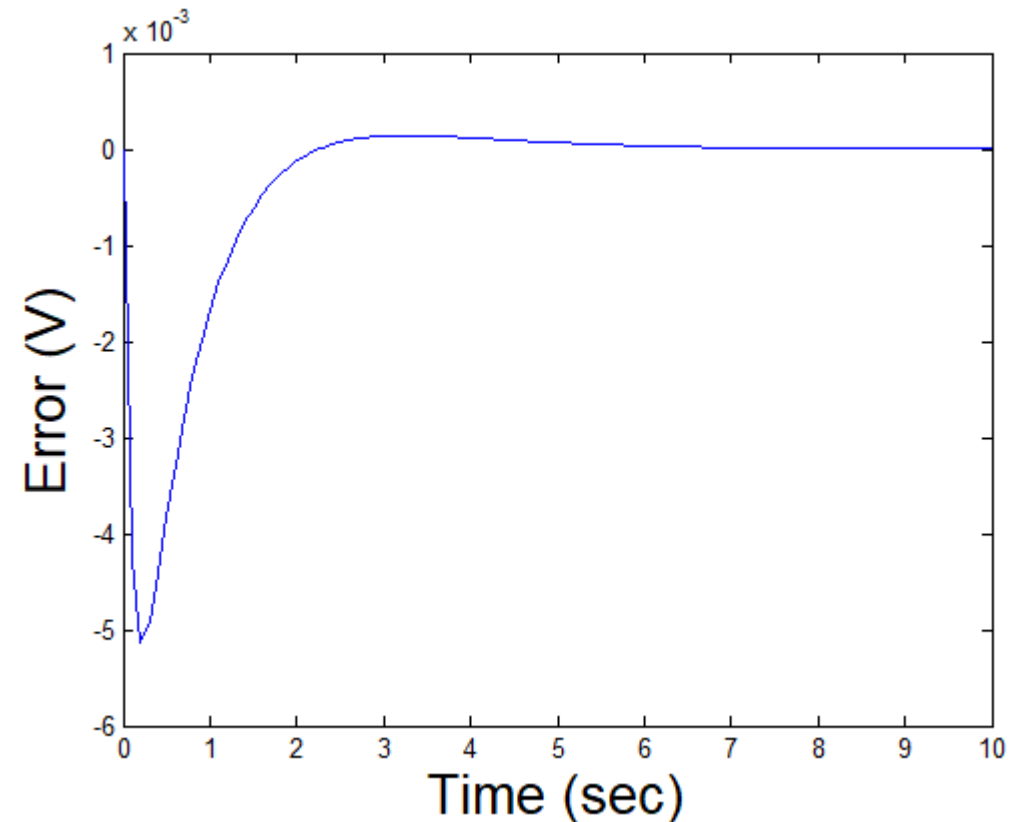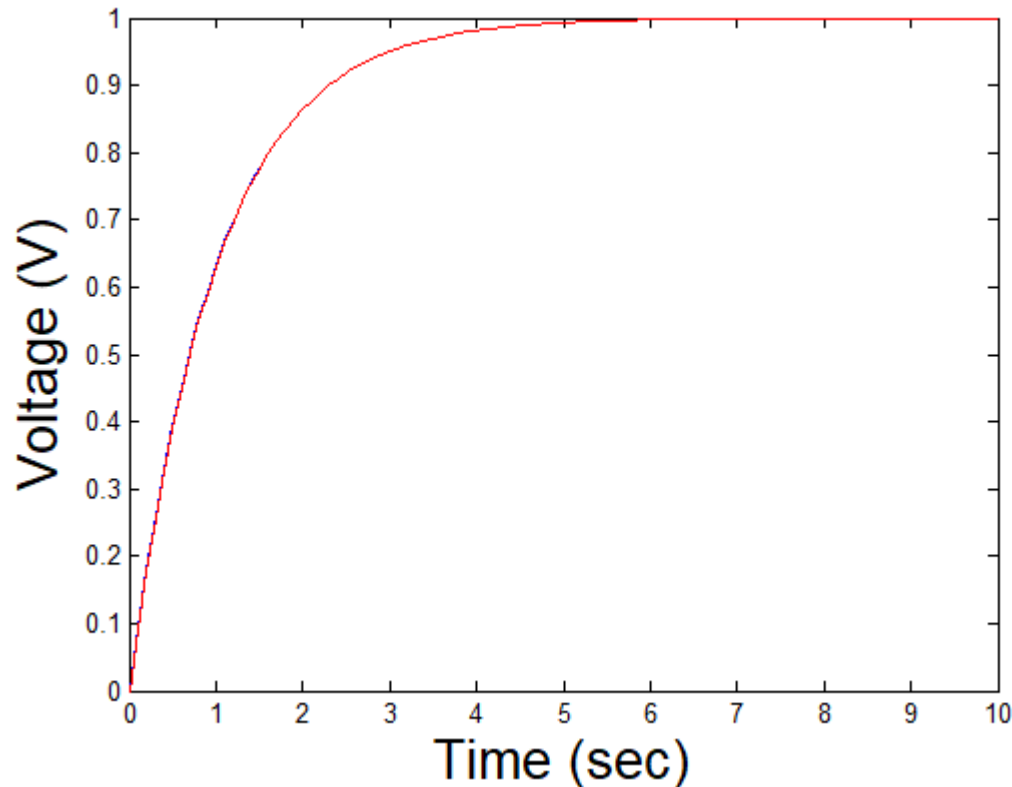- Ten times shorter time spacing
 - The difference becomes almost invisible.
 - The maximum difference is smaller than that of the backward Euler.



Case) $\Delta t = 0.01$ with Gear's method

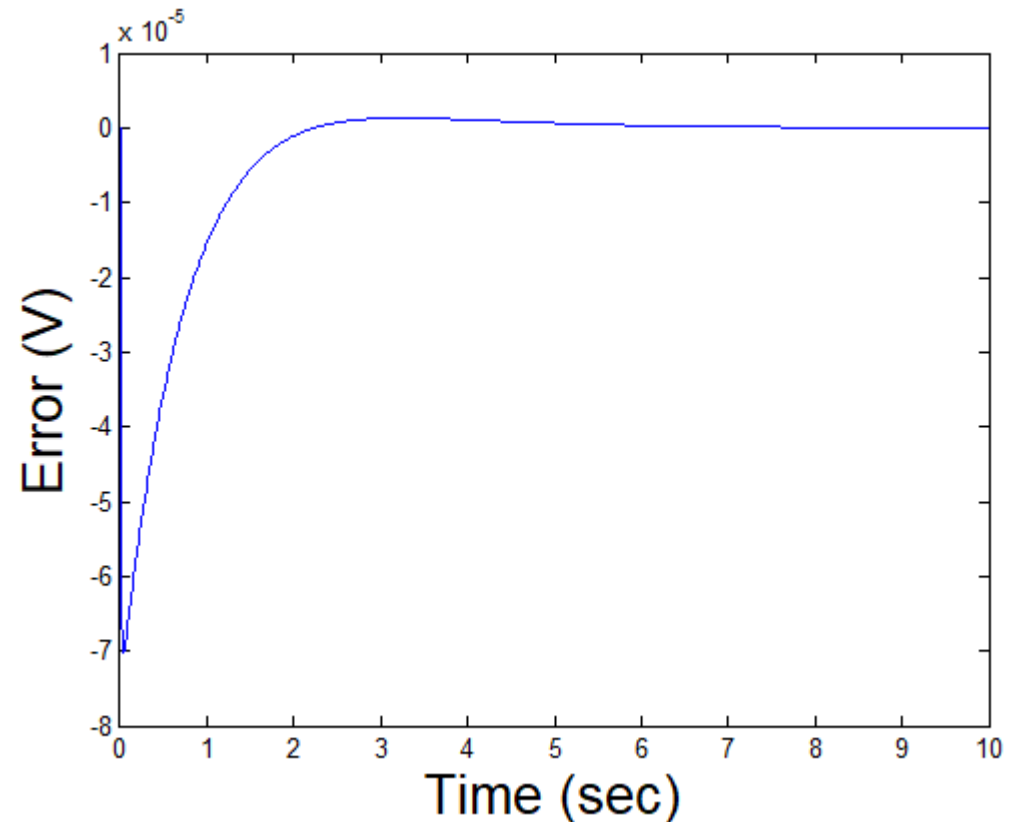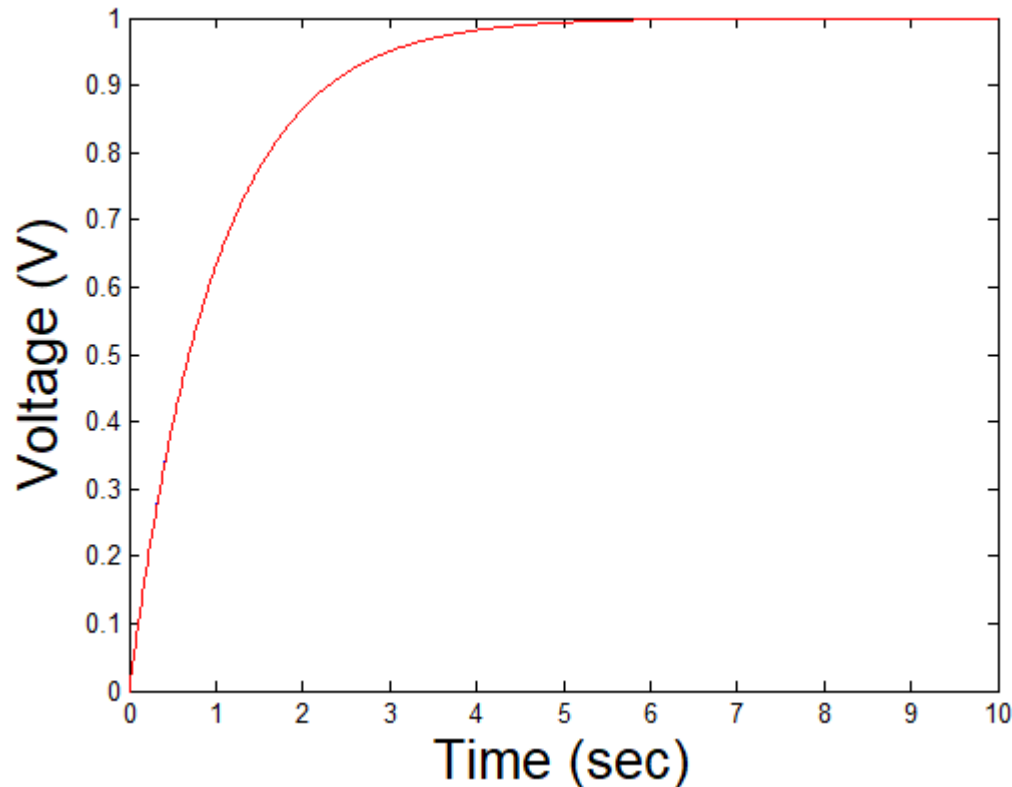- Ten times shorter time spacing, again
 - Much smaller difference is obtained.
- In summary, the error is rapidly decreasing with a smaller Δt .



Sinusoidal voltage source



- Apply a sine wave with its amplitude of 1 V.
 - The frequency is 1 Hz.
 - Then, the amplitude of V_X should be $\frac{1}{\sqrt{1+(2\pi)^2}}$ V. (0.15718 V)
 - Investigate the amplitude with various Δt values.

$$(1.5 + \Delta t)V_X(t_i) = 2V_X(t_{i-1}) - 0.5V_X(t_{i-2}) + \Delta t \sin 2\pi t$$

$$(1 + \Delta t)V_X(t_i) = V_X(t_{i-1}) + \Delta t \sin 2\pi t$$

Case study) $\Delta t = 0.01$

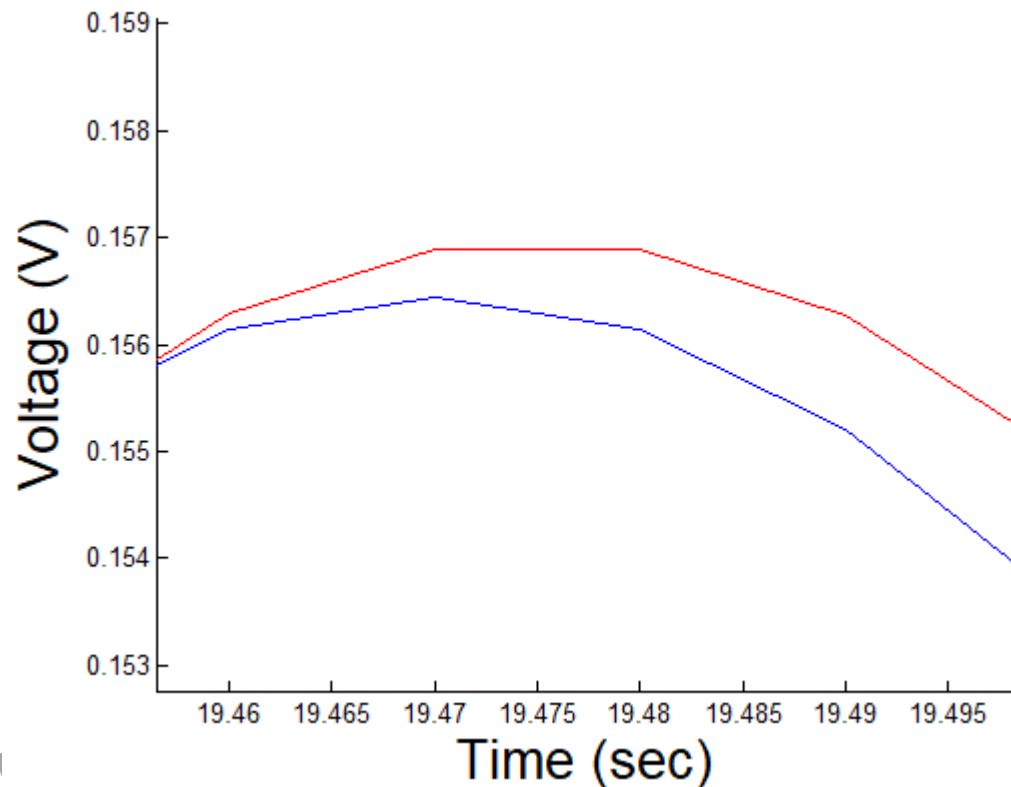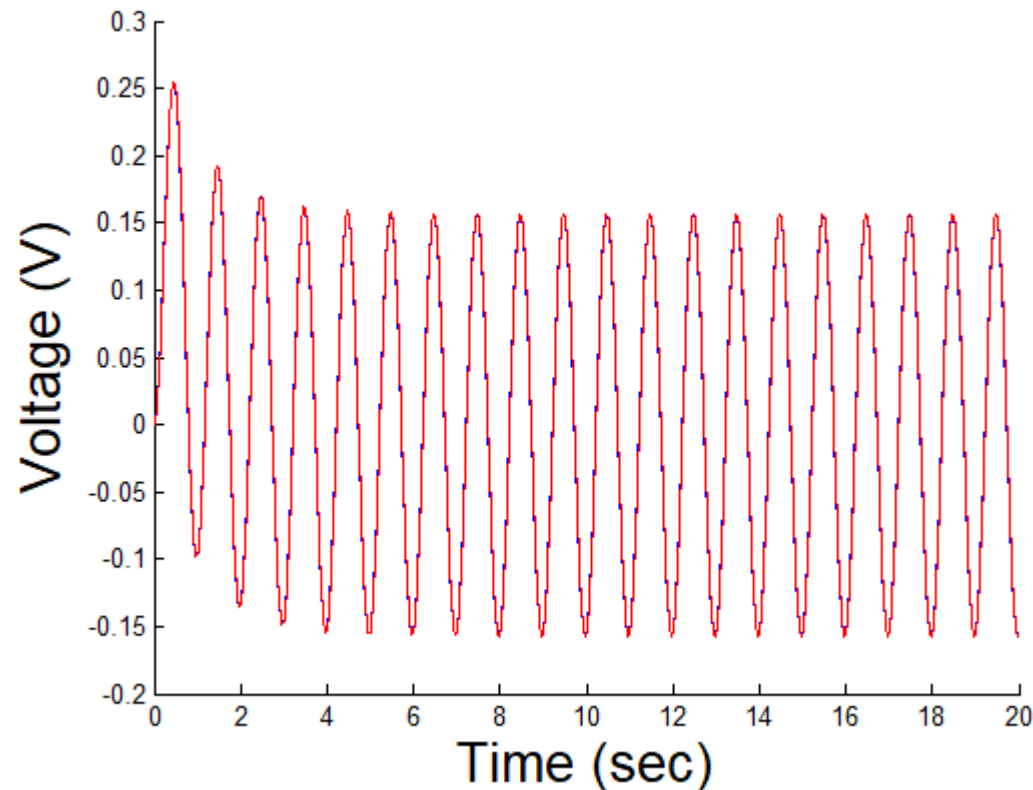- 100 points in a period (Sufficiently fine)
 - 20 cycles are passed. (Sufficiently stabilized)
 - Gear's method predicts a larger amplitude, close to 0.15718 V.



Homework#12

- Due: AM08:00, October 24

- Problem#1

- Solve the following equation:

$$I_0 \left[\exp(V_X - V_{in}(t)) - 1 \right] + C \frac{dV_X}{dt} = 0$$

- Assume that $I_0 = C = 1$.
 - Initially, the applied voltage is zero.
 - Then, apply a sinusoidal voltage source to $V_{in}(t)$. Change the amplitude and frequency.

Thank you for your attention!